

# Chapter 27: Circuits

Rylan Polster

December 12, 2020

## General

### Quantities

$R$  = resistance

$i$  = current

$\mathcal{E}$  = electromotive force (EMF)

$V_{AB}$  = terminal voltage

## 1 Single-Loop Circuits

**Loop Rule** The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero.

**Resistance Rule** For a move through a resistance in the direction of the current, the change in potential is  $-iR$ ; in the opposite direction it is  $+iR$ .

**EMF Rule** For a move through an ideal emf device in the direction of the emf arrow, the change in potential is  $+\mathcal{E}$ ; in the opposite direction it is  $-\mathcal{E}$ .

### Terminal Voltage and Internal Resistance

$$V_{AB} = \mathcal{E} - iR \quad (1)$$

## 2 Resistors in Parallel and in Series

### Resistance In Parallel

$$R_{\text{eq}} = \sum_{j=1}^n \frac{1}{R_j} \quad (2)$$

### Resistance In Series

$$R_{\text{eq}} = \sum_{j=1}^n R_j \quad (3)$$

## 3 The Ammeter and the Voltmeter

**Ammeters** Ammeters must be placed in series with the component whose current is being measured. The ammeters should have a resistance that is as low as possible ( $R_{\text{ammeter}} \approx 0\Omega$ ).

**Voltmeters** Voltmeters must be placed in parallel with the component whose voltage is being measured. The voltmeter should have a resistance that is as high as possible ( $R_{\text{voltmeter}} \approx \infty$ ).